

TUTORIAL: Phase Locked Loops

Greg Armstrong (Integrated Device Technology, Inc.)

March 18th, 2019






Outline

- Phase Locked Loops (PLL)
 - Principle
 - Response To Injected Noise

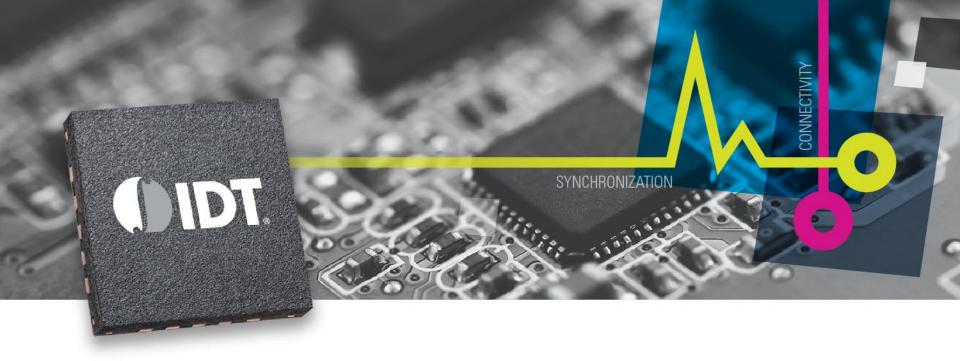- PLL Operation Modes
 - Locked, holdover and freerun
- PLL with 2 inputs








Phase Locked Loops (PLL)



PLL: Working principle

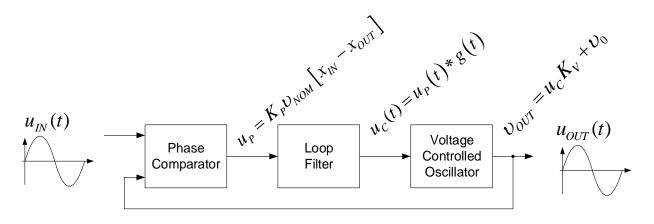

$$u_{IN}(t) = A \cdot \sin\left\{2\pi \upsilon_{NOM} \left[t + x_{IN}\left(t\right)\right]\right\} = A \cdot \sin\left\{2\pi \upsilon_{IN}\left(t\right) + \varphi_{0,IN}\right\}$$


$$u_{OUT}(t) = A \cdot \sin \left\{ 2\pi \upsilon_{NOM} \left[t + x_{OUT} \left(t \right) \right] \right\} = A \cdot \sin \left\{ 2\pi \upsilon_{OUT} \left(t \right) + \varphi_{0,OUT} \right\}$$

- A phase lock loop (PLL) is a control system that generates an output signal whose phase is related to the phase of an input signal
 - Bringing the output signal back to the input signal for comparison is called a feedback loop
- By keeping the input and output phase in lock, this implies that the input and output frequencies are the same as well
- PLLs generally generate an output frequency that is a multiple, or even a fractional multiple, of the input frequency
 - May requires an integer, or fractional, divider on the feedback
 - May require an integer, or fractional, divider on the input as well





PLL: Phase Comparator

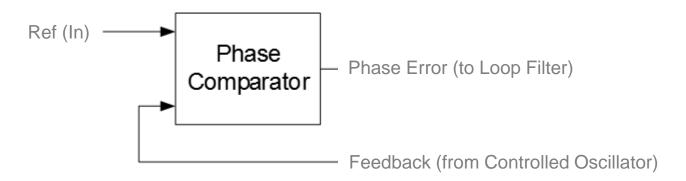

- The Phase Comparator establishes the "error" between the reference input and the clock output; using a feedback
- Most Digital PLLs (DPLLs) use a Time to Digital Converter (TDC) and Phase Frequency Detector (PFD) to measure the phase of the two clocks and produce a digital word representing the error
 - TDC can be looked at as a timestamper
- The TDC timestamps the reference and feedback edges, and the PFD mathematically tracks the phase offset between the selected reference and feedback clocks
- The measured phase difference can go well beyond 1 period, or Unit Interval (UI), of the reference and feedback clocks; thus, the phase comparator must be able to measure over a large range of multiple input/feedback clock periods
 - Various telecom standards define a jitter & wander tolerance requirement the widest is defined is 18µspp
 - For example, if the input clock has a nominal period of 8ns (125 MHz), then the jitter tolerance requirement equates to ± 1125 UI










PLL: Loop Filter

Loop Control Signal (to Controlled Oscillator) Phase Error (from Phase Comparator) Filter

- The phase error is processed by the loop filter (LF)
 - LF is a combination of proportional and integral (PI) control, which generates a control signal for controlling the oscillator
- The LF determines the bandwidth (BW) of the PLL
 - Other functionality, such as phase slope limiting (PSL), locking range, and holdover functionality may be done as well
- Phase corrections mainly done through proportional path, along with any PSL
- Frequency offset, or drift corrections, is done through the integrator path, including damping (i.e. gain peaking control)






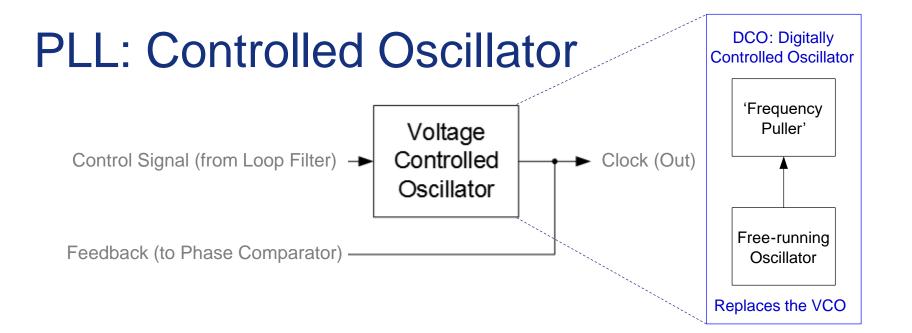

- The controlled oscillator uses the control signal to speed up or slow down the output clock
- Most Digital PLLs replace the Voltage Controlled Oscillator (VCO) by a Digitally Control Oscillator (DCO) consisting of:
 - a free-running crystal oscillator (XO)
 - A digital synthesizer which pulls the frequency up or down using a Control Signal from loop filter (a digital word representing a fractional frequency offset (FFO))




PLL: Phase-time deviation x(t)

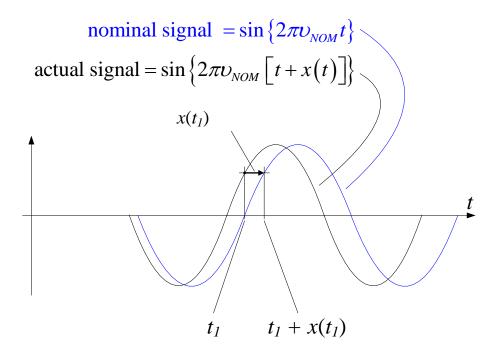

Note:


Phase-time x = random component onlyTime Error TE = random and deterministic components

PLL: Response to Injected Noise

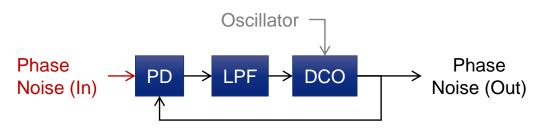


$$X_{OUT}(t) = X_{IN}(t) * h_{IN}(t)$$

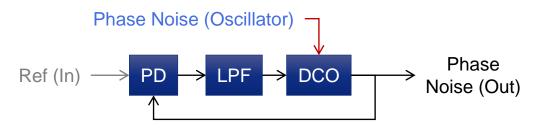 $X_{OUT}(s) = X_{IN}(s) \cdot H_{IN}(s)$
where $h_{IN}(t) = \text{impulse response}$
 $H_{IN}(s) = \text{transfer function} = \text{Laplace}\{h_{IN}(t)\}$




$$\begin{aligned} x_{OUT}\left(t\right) &= x_{OSC}\left(t\right) * h_{OSC}\left(t\right) \\ X_{OUT}\left(s\right) &= X_{OSC}\left(s\right) \cdot H_{OSC}\left(s\right) \\ \text{where } h_{OSC}\left(t\right) &= \text{ impulse response} \\ H_{OSC}\left(s\right) &= \text{ transfer function } = \text{Laplace}\left\{h_{OSC}\left(t\right)\right\} \end{aligned}$$

PLL is a low-pass filter for input noise

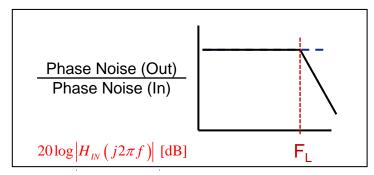


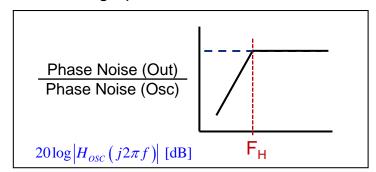
PLL is a high-pass filter for oscillator noise



PLL: Jitter & Wander filtering

- What is jitter/wander?
 - Noise or other disturbances on the clock when compared to an ideal reference
 - Jitter = short-term variations
 - Wander = long-term variations
 - ITU-T G.810 defines noise frequencies <10Hz as wander and frequencies >10Hz as jitter
- The function of a PLL is to attenuate jitter and transfer wander
 - In other words, tolerate noise at the input without losing lock to the reference

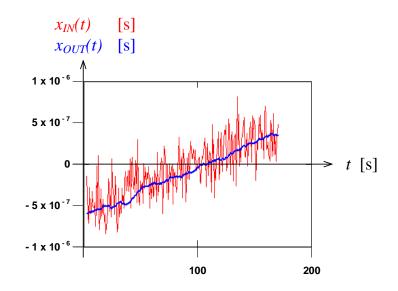


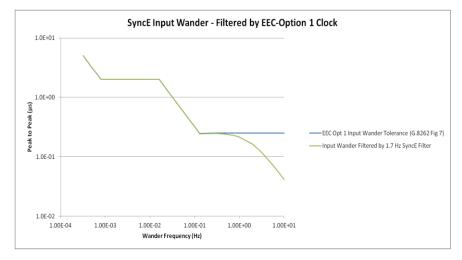







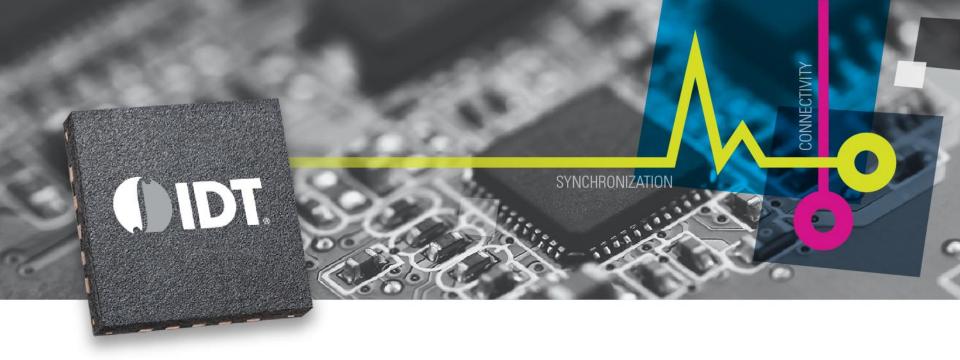

PLL Operation Modes




PLL Modes: Locked, holdover and freerun

- Locked mode: clock has a valid input signal, PLL loop is closed, i.e. switch is in position 1.
- Freerun & holdover modes: no valid input signal is detected, controller switches to position
 2, clock becomes an autonomous synchronization source.

Holdover: memory MEM remembers last locked mode frequency

Freerun: value in the holdover memory is invalid or outdated

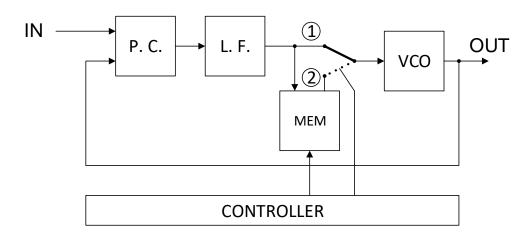After entry into freerun or holdover mode, frequency is subject to ageing drift and to the influence of temperature.






PLL Modes: Holdover @ constant temperature

Fractional frequency:

$$y(t) = y_0 + D \cdot t$$

where y_0 = initial frequency offset

D =frequency drift rate (constant)

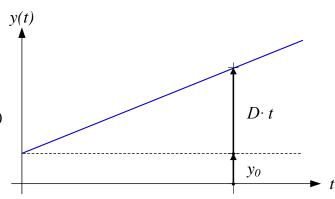


Time error:


$$x(t) = x_0 + y_0 \cdot t + \frac{D}{2} \cdot t^2$$

where x_0 = initial phase offset

 y_0 = initial frequency offset

D =frequency drift rate (constant)

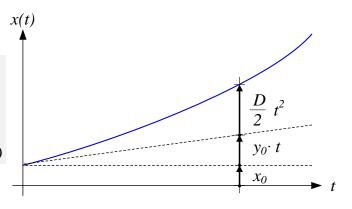


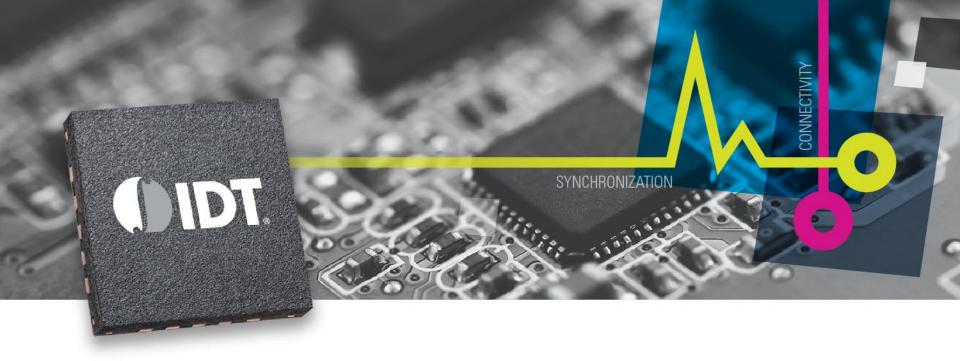



PLL with 2 Inputs



Combining two PLLs

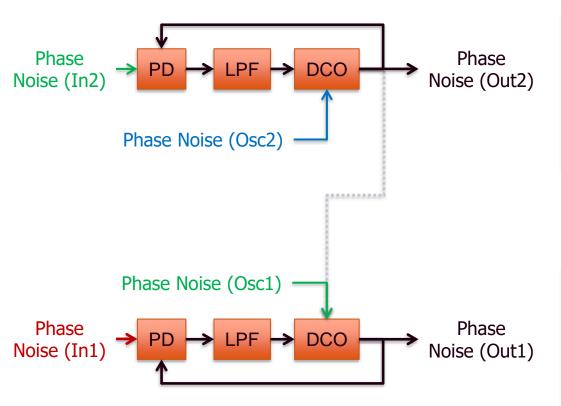

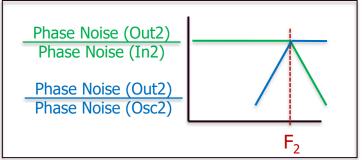


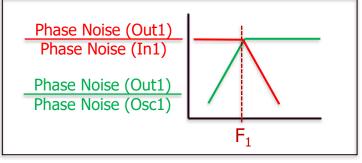






Two PLLs: Response to Injected Noise

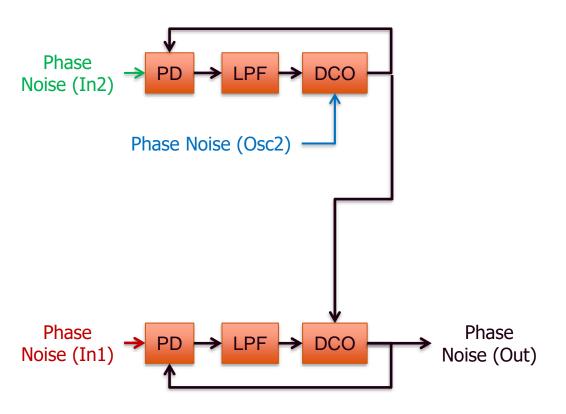

Band-pass filter for In2 Noise to Out

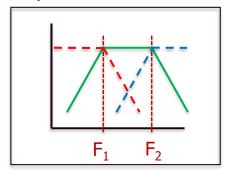






16


Two PLLs: Spectral densities


Three spectral densities (phase-time) ...

... combined by the 2-input PLL, ...

... result in this out spectral density:

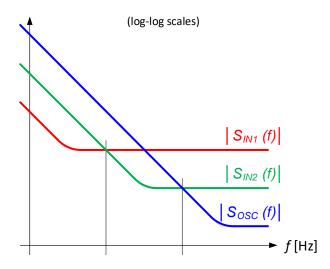

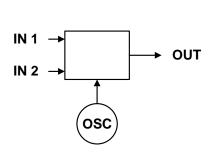

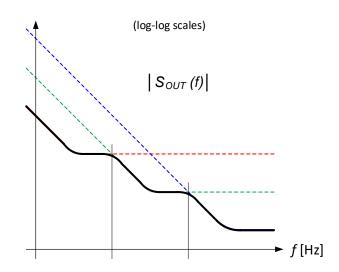





Two PLLs: Applications

GNSS & Cesium clock in enhanced Primary Reference Time Clocks (ePRTC)

PTP & SyncE in boundary clocks (T-BC) and slave clocks (T-TSC)

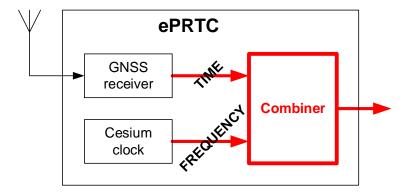Note: PLL with 2 inputs is not the only way of combining 2 references




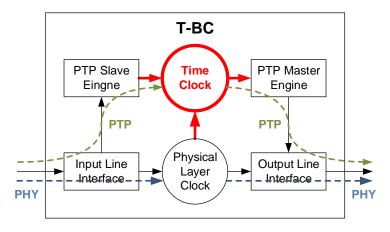






T-BC: Response to Injected SyncE Noise

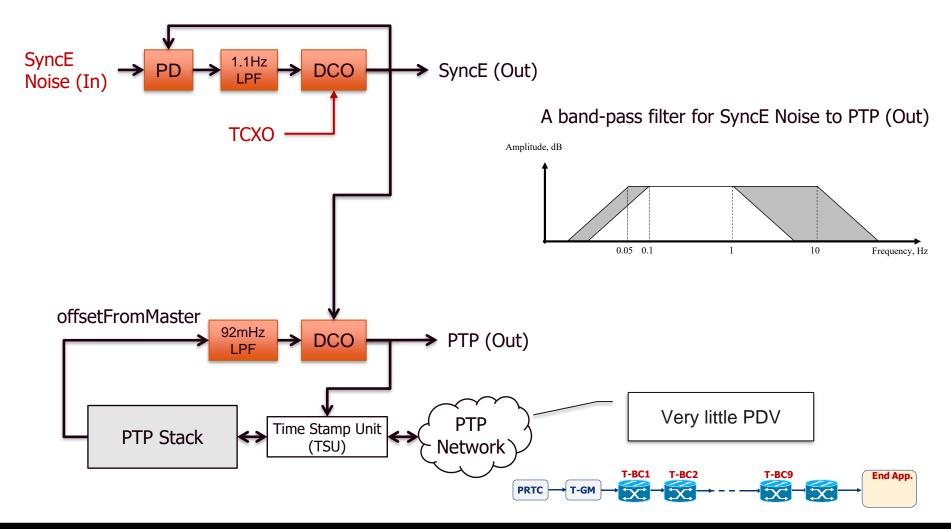





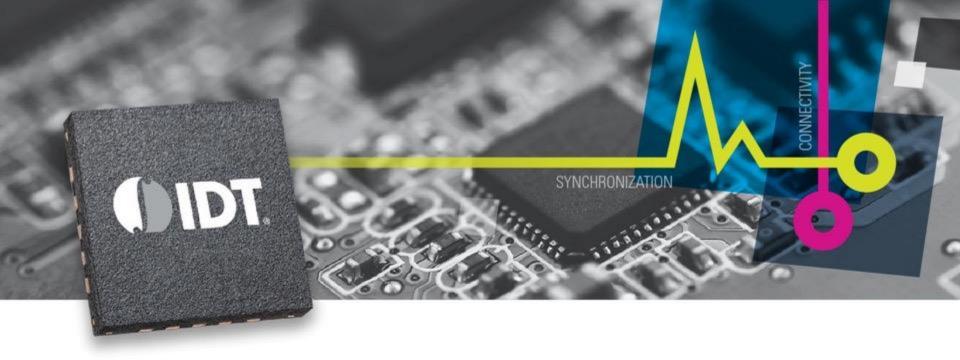

Thank You

Analog Mixed Signal Product Leadership in Growth Markets





